

Memristors HW2

Chris Shakkour, 208157826, christian.s@campus.technion.ac.il

Nadi Najjar, 211610704, nadi.najjar@campus.technion.ac.il


Contents

Question 1 – Multi-level cells (MLC)	2
Part-a	Error! Bookmark not defined.
Part-b	Error! Bookmark not defined.
Part-c	Error! Bookmark not defined.
Part-d	Error! Bookmark not defined.
Question 2 – stateful logic (MAGIC)	6
Part-a	6
Part-b	6
Part-c	6
Part-d	9
Part-e	10


Question 1 – Multi-level cells (MLC)

Part a :

Circuit –

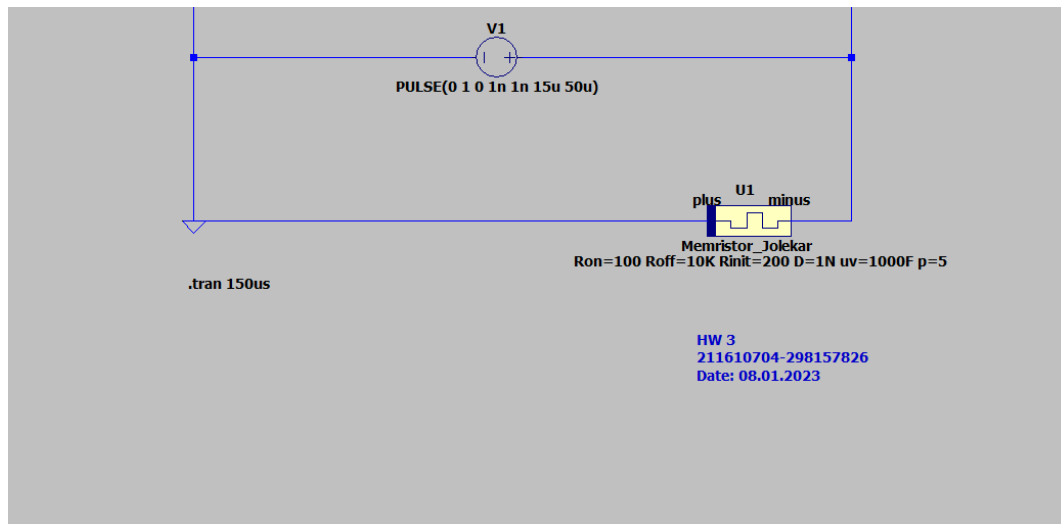

Plot –

 

Explanation –

Green graph : We can see that the input voltage is a pulse train that swings between 0 and 1.

Blue graph : We get the maximum value of the current when we are at 200ohm resistance (lowest) and then the current decreases and the state gets lower, resistance increases.


Red graph : from the graph we can see that the state variable is not linear and it decreases in each voltage pulse as expected from the tutorial.

Light blue : The resistance increases with each pulse, in a result of that the state variable decreases.


There is 4 levels of resistance – 200ohm, 5.4Kohm, 7.6Kohm, 9.3Kohm.

Part b –

Circuit –

 

Plot –

 


Explanation –


In order to make the 4 levels of resistances uniform in the range $[R_{ON}, R_{OFF}]$ we need to use these pulse durations: $Pulse1_width \approx 6\mu s \Rightarrow R_{on} \rightarrow 3.3K\Omega$ $Pulse2_width \approx 16.9\mu s \Rightarrow 3.3K\Omega \rightarrow 6.59K\Omega$ $Pulse3_width \approx 32.2\mu s \Rightarrow 6.59K\Omega \rightarrow 9.9K\Omega$

Part c –

Circuit –

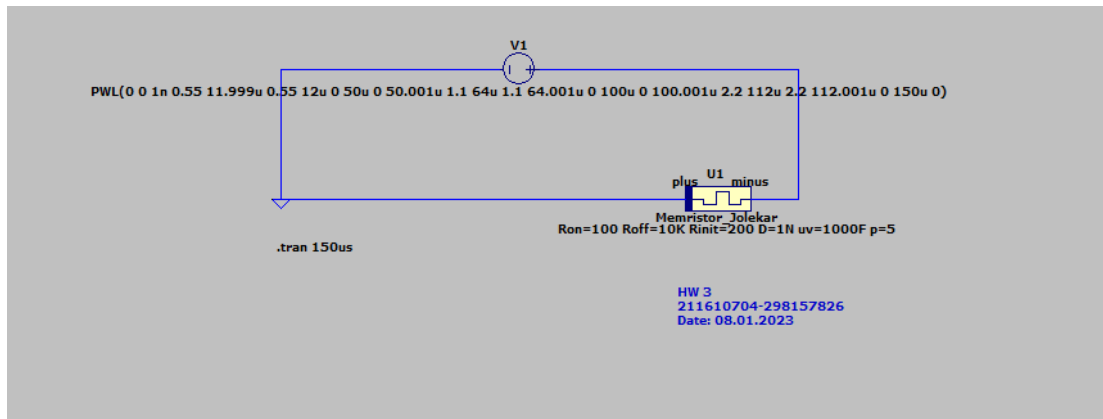

Plot –

 


Explanation –


To get an approximately uniform resistance, We chose $V1=0.55V$ for $10.999\mu s$ and $V2=1.1V$ for $13.999\mu s$ and $V3=2.2V$ for $11.999\mu s$.

Part d –

Circuit –

 

Plot –

 

1st graph is the current that passes through the memristor , 2nd graph is the Resistance , 3rd graph is the Memristor state, 4th graph is the voltage the falls on the memristor and 5th graph is the input voltage.


We used step param to determine which R_{in} to choose that will give us uniform resistance (200ohm, 3.32Kohm, 6.6Kohm, 10Kohm) and we found that $R_{in} = 5Kohm$ will give us this result.

Question 2 – stateful logic (MAGIC)

$$\frac{dx}{dt} = \begin{cases} e^{a_1 - x} & v > V_f \\ 0 & V_r \leq v \leq V_f \\ -e^{a_2 + x} & v < V_r \end{cases}$$

$$R(x) = \begin{cases} R_{ON} & x \geq 0 \\ R_{OFF} & x < 0 \end{cases}$$

Parameter	Value
R_0	1k
R_1	10
a_1	5
a_2	5
V_f	1.2
V_r	-0.5

 

Part-a

Writing down the constraints will lead to the following assumption:

$$\text{when } \{in_1 = 0, in_2 = 0\} \rightarrow V_{out} < V_{t_{off}}$$

$$(1) V_0 * 2 * \frac{R_{on}}{R_{on} + R_{on}} < V_{t_{off}} \rightarrow V_0 < |V_f|$$

$$\text{when } \{in_1 = 1, in_2 = 0\} \text{ or } \{in_1 = 0, in_2 = 1\} \text{ or } \{in_1 = 1, in_2 = 1\} \rightarrow V_{t_{off}} < V_{out}$$

$$(2) 2 * |V_r| < V_0 < |V_r| * \frac{R_{off}}{2R_{on}}$$

Part-b

We plug the numbers from the table above and get:

$$V_0 < 1.2$$

$$1 < V_0 < 25$$


In the end the constraint is:

$$1 < V_0 < 1.2$$

We choose $V_0 = 1.1$

Part-c

Following schematics

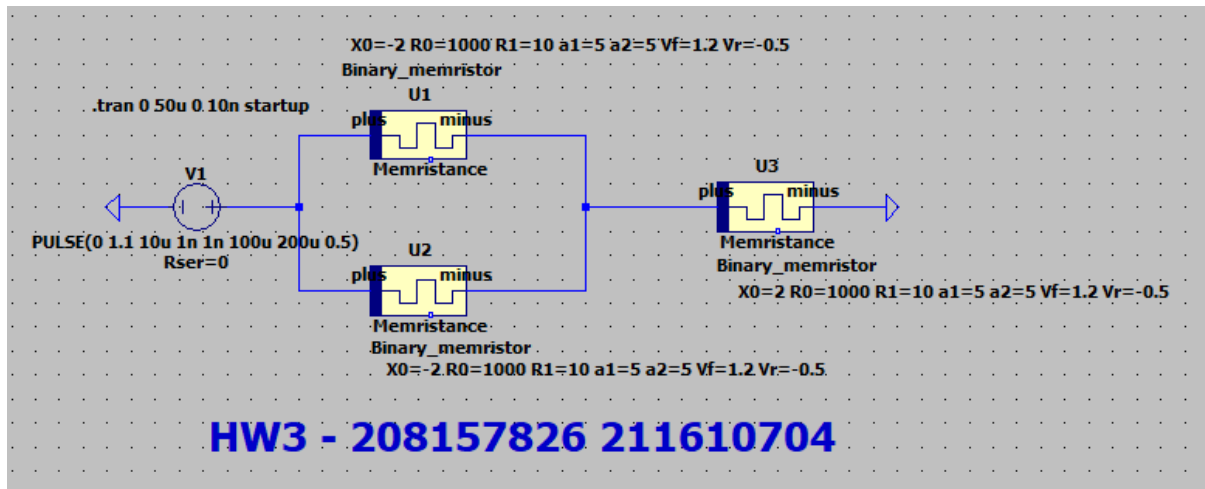


Source voltage in **Green**: $V(n001)$: notice it is negative this is due to the polarity of the memristors.

Resistance of U1 in **Purple**: $(V(n001)-V(n002))/I(U1)$


Resistance of U2 in **Red**: $(V(n001)-V(n002))/I(U2)$

Resistance of U3 in **Gold**: $V(n002)/I(U3)$


a. $\{in_1 = R_{on}, in_2 = R_{on}\}$

 


b. $\{in_1 = R_{on}, in_2 = R_{off}\}$

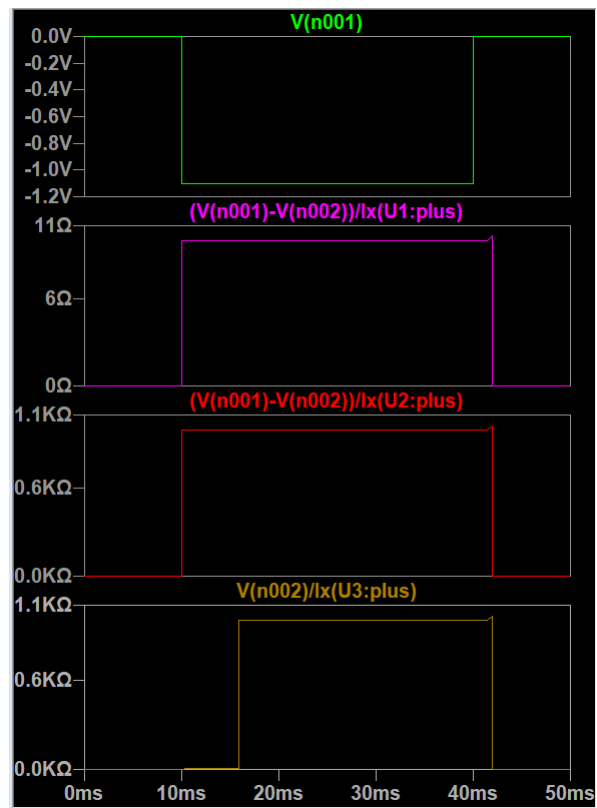


c. $\{in_1 = R_{off}, in_2 = R_{off}\}$

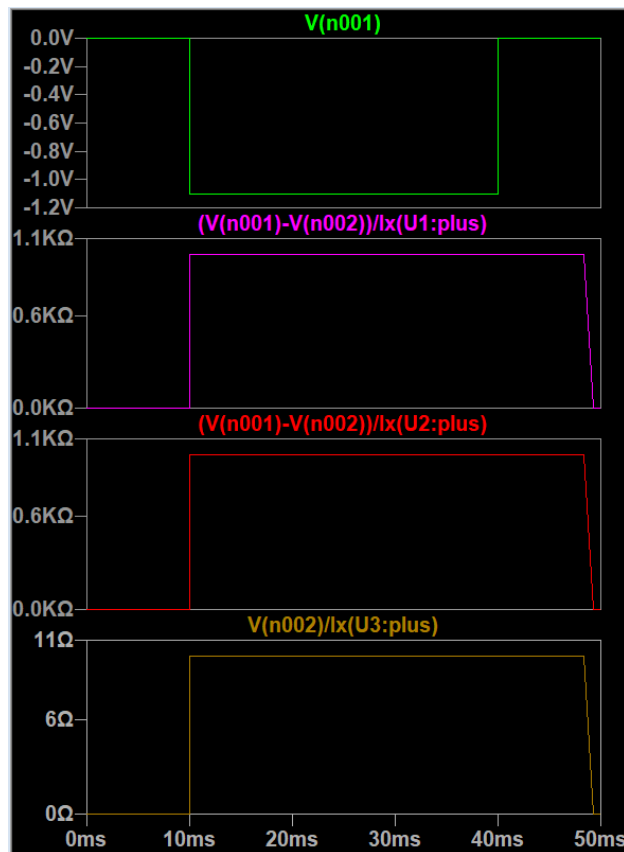

Part-d

 

Part-e

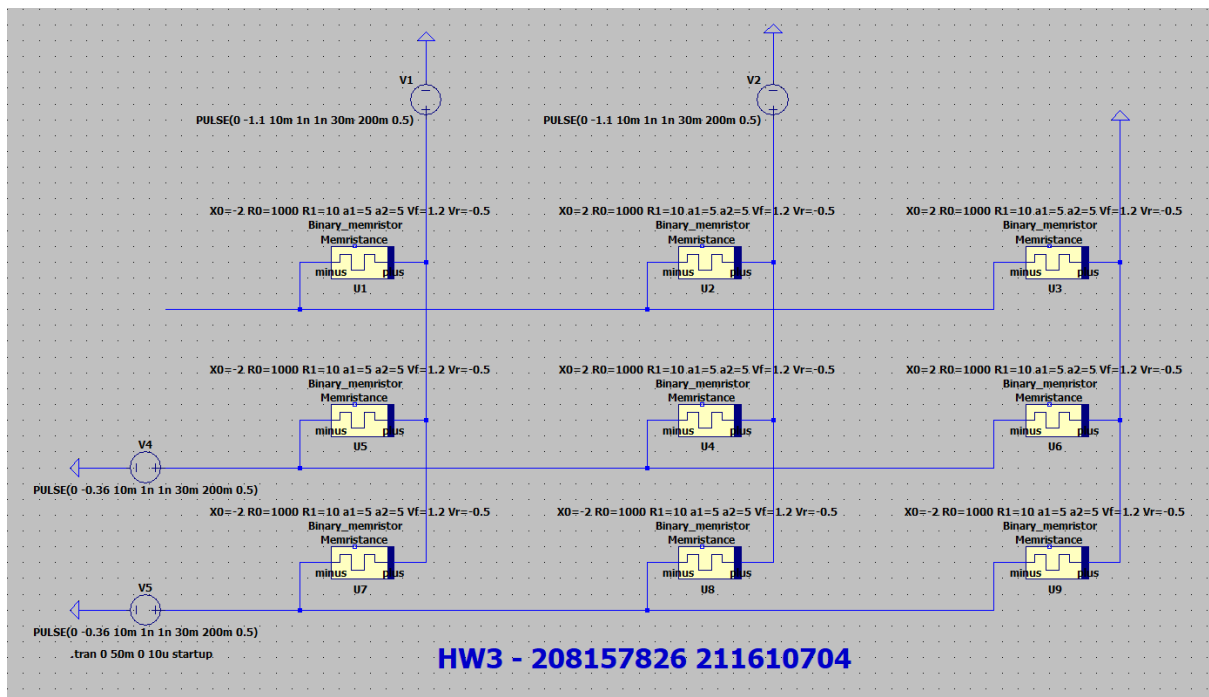


Source voltage in **Green** (V0)

Resistance of U3 in **Blue**

Resistance of U2 in **Red**

Resistance of U1 in **Cayan**

First Row memristors :

 


Source voltage in **Green** (V0)

Resistance of U6 in **Blue**

Resistance of U4 in **Red**

Resistance of U5 in **Cyan**

Second Row memristors:

 

Source voltage in **Green** (V0)

Resistance of U9 in **Blue**

Resistance of U8 in **Red**

Resistance of U7 in **Cayan**

third Row memristors:

